



## FACULTY OF ENGINEERING AND TECHNOLOGY

### Department of Computer Engineering

#### EEF 362: ANALOG ELECTRONICS

**LEVEL AND SEMESTER:** Undergraduate L300, Second semester

**Credit value:** 3

#### LAB 3 REPORT

#### TITLE: ZENER DIODE CHARACTERISTICS

**Group number:** Group 5

**Subgroup number:** Subgroup 4

**Group members(name and matricule number)**

- |                               |          |
|-------------------------------|----------|
| 1. NGUEDIA JEATSA Joyce Grace | FE21A263 |
| 2. NGONCHI RAMATOU Yollande   | FE21A260 |
| 3. NGOBA Steve Jones NTONG    | FE21A259 |
| 4. NGOUNG TASSA Alain Shiress | FE21A262 |

*Second semester, 2023*


## AIMS

- To measure the effects of forward and reverse biased on the Zener diode current and to construct the Zener diode characteristics
- To study a Zener voltage regulator by determining the range over which the Zener maintains a constant output voltage.

## OBJECTIVES

- Identify and characterize the Zener diode and to differentiate it from the pn junction diode;
- Give advantages of Zener diode regulator over regulators
- Manufacture a proper Zener voltage regulator for dedicated applications
- Understand the specific role played by a Zener diode in electronic devices

**Figure 1: line regulator**

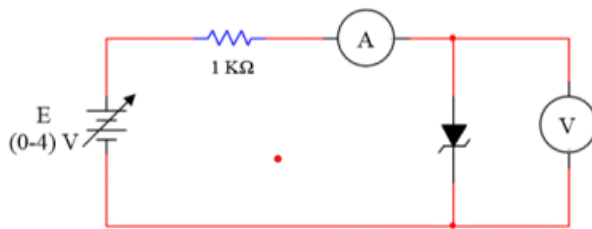

*Figure (1)*


**i. Forward biased**

E(v)	0	1	2	3	4	5	6	7	8	9
V <sub>f</sub> (v)	0.00	0.70	0.74	0.76	0.77	0.78	0.78	0.79	0.79	0.79
I <sub>f</sub> (mA)	0.00	0.40	1.20	2.32	3.28	4.35	5.27	6.04	6.96	7.90

**ii. Reversed biased**

E(v)	0	2	4	6	8	10	12	13	14	15
V <sub>z</sub> (v)	0.00	2.15	4.24	6.13	3.56	8.67	8.71	8.73	8.74	8.76
I <sub>z</sub> (mA)	0.00	0.00	0.00	0.00	0.00	1.34	3.22	4.16	4.72	6.17

**Figure2: load regulation**

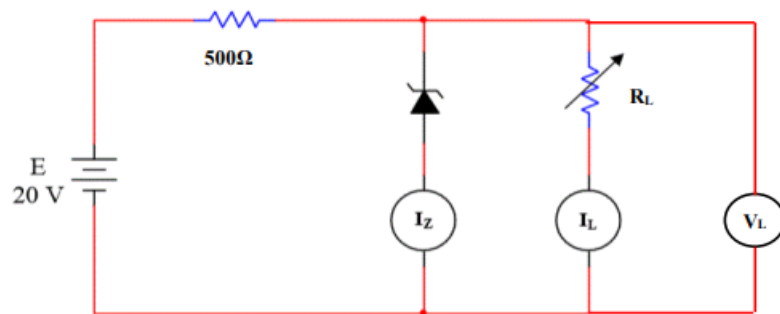

**Figure (2)**

i.

$R_L(k\ \text{ohms})$	1	2	3	4	5	6	7
$I_Z(\text{mA})$	0.72	5.00	6.45	7.23	9.40	7.92	9.42
$I_L(\text{mA})$	8.86	4.50	3.00	2.25	1.80	1.49	1.35
$V_L(\text{v})$	8.73	8.85	8.86	8.89	8.94	8.92	8.95